



**RAJARATA UNIVERSITY OF SRI LANKA  
FACULTY OF APPLIED SCIENCES**


BSc in Applied Sciences  
Second Year - Semester I Examination – May/July 2022

**PHY 2103 – ELECTRONICS I**

**Time: One (01) hour**

**Answer only two Questions.**

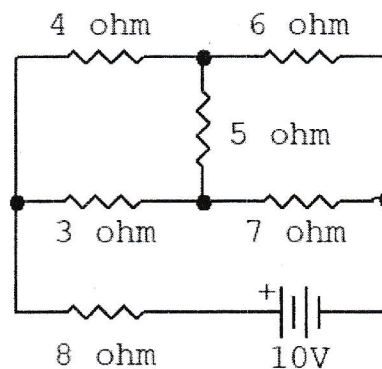1. a) Using the Kirchhoff's rules, determine the current through the  $5\ \Omega$  resistor in the network shown in the following figure.



(10 marks)

- b) Given, for silicon at 300 K temperature, intrinsic carrier concentration ( $n_i$ ) is  $1.5 \times 10^{10}\text{ cm}^{-3}$ , electron mobility ( $\mu_e$ ) is  $1250\text{ cm}^2\text{V}^{-1}\text{s}^{-1}$ , the hole mobility ( $\mu_h$ ) is  $600\text{ cm}^2\text{V}^{-1}\text{s}^{-1}$  and the number of Silicon atoms per  $\text{cm}^3$  is  $5 \times 10^{27}$ .


Calculate the conductivity of silicon under following conditions.

- i. In intrinsic condition at a room temperature of 300 K.
- ii. With a donor impurity of 1 in  $10^9$  Silicon atoms.
- iii. With an acceptor impurity of 1 in  $6 \times 10^7$  Silicon atoms.
- iv. With both the above impurities present simultaneously.

(10 marks)


**Contd.**

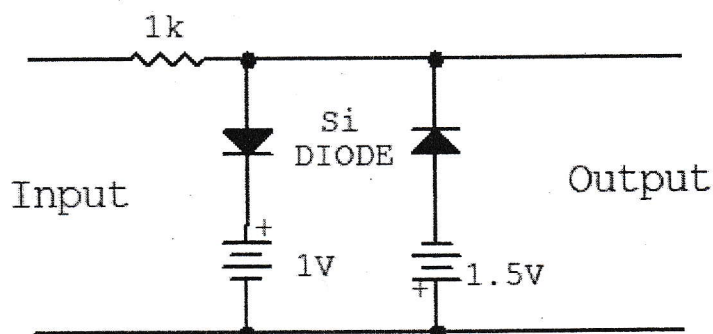- c) Illustrate the output signal produced by the clipper circuit shown in the figure below, for a 5V (p-p) sinusoidal input signal.



(05 marks)

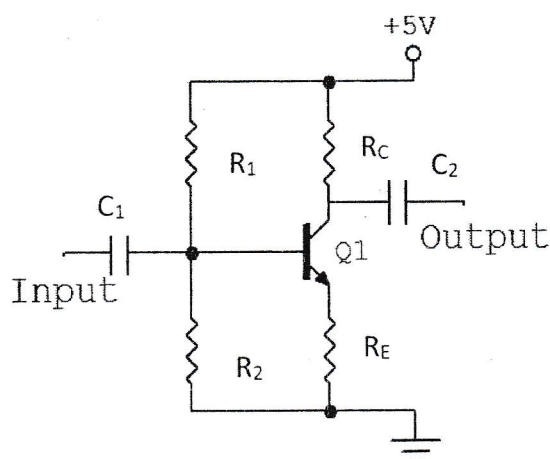2. Use the given circuit to perform the following calculations.



- Can this circuit be used as a class A amplifier with a 4V collector voltage ( $V_C = 4V$ )?
- To which class of amplifiers could this circuit belong as it was shown? Explanation should be based on the Q point value ( $V_C = 4V$ ).
- Calculate the resistance  $R_C$  and the base current  $I_B$  when the collector current is 2mA and current gain ( $\beta$ ) is 150.
- Determine a suitable value for  $R_E$  to bias the transistor in the active region.
- Assuming  $Q_1$  is a silicon transistor, calculate suitable values for the  $R_1$  and  $R_2$  with a low input impedance.

(25 marks)


3. a) Explain why an op-amp needs a feedback loop when it is used in circuits other than in a comparator circuit.

(05 marks)

- b) What are the two rules used in Op-amp circuits? Explain how those two differ from actual behaviour.


(05 marks)

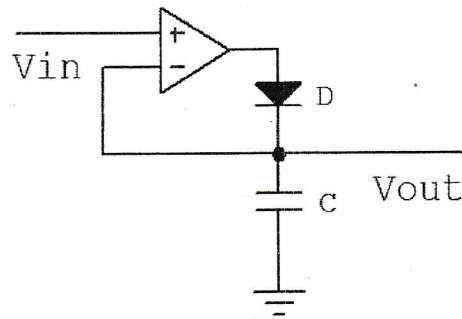- c) Explain the functionality of the op-amp peak detector circuit shown below.



(05 marks)

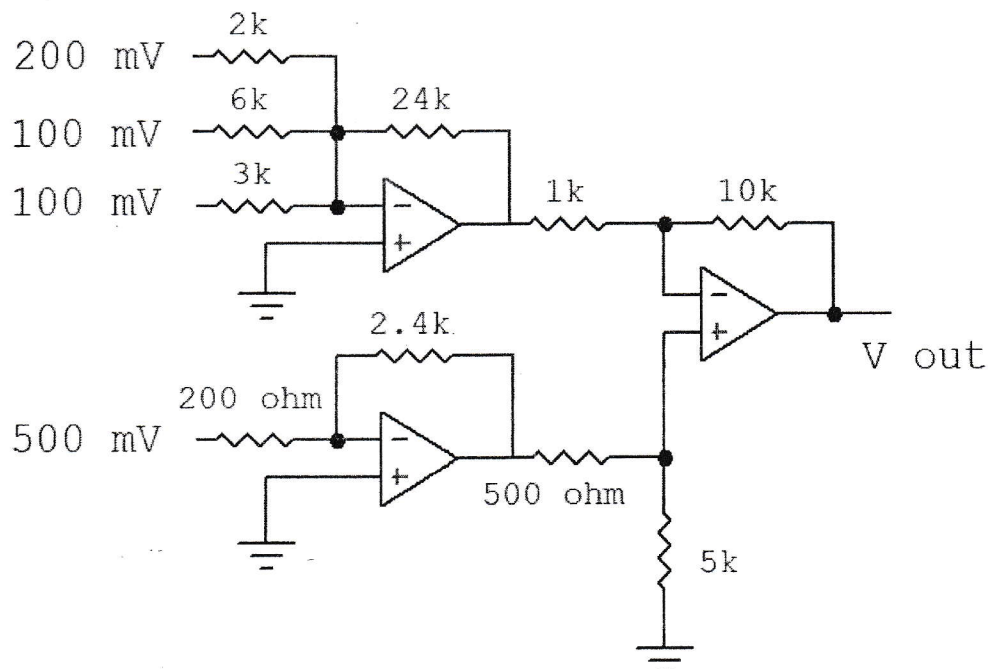- d) Calculate the output voltage ( $V_{out}$ ) for the following circuit.



(10 marks)

End.