



**RAJARATA UNIVERSITY OF SRI LANKA  
FACULTY OF APPLIED SCIENCES**

**B.Sc. (General) Degree in Information & Communication Technology  
First Year Semester I Examination – April / May 2015**


**ICT 1303 – Basic Electronics and Digital Logic Design**

---

**Instructions for candidates**

- This is a closed book examination.
- There are **FOUR (4) pages** in the question paper.
- Time allowed will be **THREE (3) hours**.
- Question paper consists of **SIX (6) questions**.
- **Answer any FIVE (5) questions**
- All questions carry equal marks.

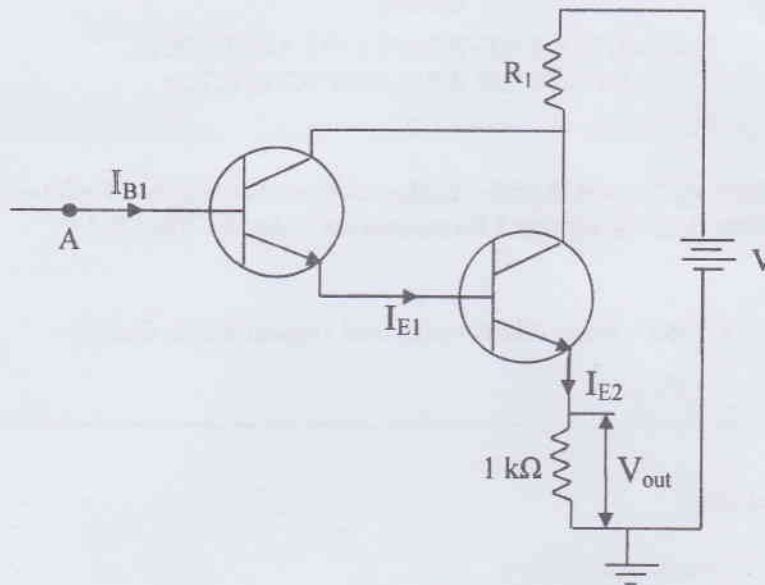**Q1.** The Following circuit diagram shows a use of two Bipolar Junction Transistors (BJT) in current amplification. This is known as Darlington pair circuit, where the output current ( $I_{E1}$ ) of the first transistor is fed as the input current for the second transistor.



- 1) If the current gain  $\beta = 100$  for both transistors, find the output current ( $I_{E2}$ ) when the input current  $I_{B1} = 1 \mu\text{A}$ . **(6 Marks)**
- 2) Find the output voltage ( $V_{\text{out}}$ ) across the  $1 \text{ k}\Omega$  resistor. **(4 Marks)**
- 3) If the  $V_{BE} = 0.7 \text{ V}$  for both transistors, find the voltage at point A. **(4 Marks)**
- 4) Plot the  $I_C$  vs  $V_{CE}$  graph for various values of  $I_B$  in a BJT and mark the three main biasing modes on the same graph. **(3 Marks)**
- 5) State the biasing modes the transistor should operate when it is used as an amplifier and a switch. **(3 Marks)**

**Q2.** Semiconductors have electrical conductivities that are falling between conductors and insulators.

- 1) What are intrinsic semiconductors? **(2 Marks)**
- 2) Briefly discuss the electrical conductivities of intrinsic semiconductors at room temperature (300 K) and absolute zero temperature (0 K) **(4 Marks)**
- 3) Using Si crystal as an example, explain how a p - type semiconductor is formed from an intrinsic semiconductor. **(4 Marks)**
- 4) Draw the I-V curve for a diode and mark forward bias, reverse bias and break down regions on it. **(4 Marks)**
- 5) Give electronic devices (or components) that can be used in following situations
  - a. To reduce the current flow on a circuit **(2 Marks)**
  - b. To convert AC current in to DC current **(2 Marks)**
  - c. To remove unwanted signal interferences **(2 Marks)**

**Q3.**

- 1) Convert the following Binary numbers into Hexadecimal and Octal numbers
  - a. 1101101 (2 marks)
  - b. 10110111 (2marks)
  - c. 11011 (2 marks)
- 2) What are the advantages and Disadvantages of Diode Logic Gates? (4 marks)
- 3) Design a circuit with 3 inputs (A,B,C) and 2 outputs (Y,Z) with respect to the following conditions
  - a. Y is 1 if A is 1 OR B AND C are 1
  - b. Z is 1 if B OR C is 1 but not both
  - c. Z is 1 if A AND B AND C are 1

Write the Truth table and obtain the Sum of Products (SOP) expression (4 marks)
- 4) Simplify the expression you obtained in part(3) using two Karnaugh maps and draw the simplified circuit diagram (6 marks)

**Q4.**

- 1) Draw the circuit diagrams for following Boolean expressions using minimum number of logic gates as possible. (4 marks)
  - a.  $(\overline{A+B}).(C+D)$
  - b.  $\overline{\overline{X} + \overline{Y}}$
  - c.  $\overline{X.Y} \oplus Y.Z$
  - d.  $(\overline{A.B}) + (\overline{A.B}) + (A.\overline{B}) + (A.B)$
- 2) Simplify the following expressions using theorems in Boolean algebra. (6 marks)
  - a.  $(A+C).(A.D+A.\overline{D}) + A.C + C$
  - b.  $A.\overline{B}.(\overline{A}+B)(\overline{B}+B)$
- 3) Prove the following theorems using truth tables.
  - a.  $\overline{A+B} = \overline{A}.\overline{B}$  (3Marks)
  - b.  $\overline{A.B} = \overline{A} + \overline{B}$  (3Marks)
- 4) Draw the Logical Symbols for XOR and NOR gates and write down the relevant truth tables. (4 marks)

**Q5.**

- 1) What is a multiplexer? How does it differ from a Decoder? (4 marks)
- 2) Write the truth table for a 1-bit 4 by 1 multiplexer (4 marks)
- 3) Obtain the Sum of Products (SOP) expression and draw the circuit diagram using minimum number of logic gates (4marks)
- 4) What are the differences between combinational logical components and sequential logical components (4 marks)
- 5) Draw the circuit diagram of a Gated S-R Flip-Flop using logic gates and write the truth table (4 marks)

**Q6.**

- 1) Briefly explain the functions of a binary encoder. (3 marks)
- 2) Write the truth table of an 8 to 3 binary encoder and obtain the Sum of Products (SOP) expressions for the 3 outputs. (6 marks)
- 3) What is a counter in digital electronics? (3 marks)
- 4) Design a 3 bit up counter using T flip-flops. (4 marks)
- 5) State whether the following components are combinational or sequential.
  - a. Register (1 mark)
  - b. Decoder (1 mark)
  - c. Timer (1 mark)
  - d. Comparator (1 mark)

-----End-----