

(a) (i) Describe the Physical significance of the Poynting **vector**. [06 marks]

(ii) Calculate the Poynting vector for a long straight wire of resistance R , radius a and length l , which carries a constant current I along the wire. Recall that the magnetic field at the surface of the wire is given by $B = \frac{\mu_0 I}{2\pi a}$. [16 marks]

(iii) Hence, show that the rate at which electromagnetic energy flows into the wire equals the rate of energy dissipated as joule **heat**. [08 marks]

(b) (i) Do Maxwell's equations prescribe any change in the velocity of electromagnetic waves through free space or any restriction to the frequency of oscillations in these waves? Justify your answer. [0 marks]

(ii) "Plane electromagnetic waves follow the laws of reflection just like light radiations". State whether the above statement is true or false. **Explain**. [10 marks]

(3) (a) (i) Discuss the phenomenon of resonance in series RLC circuit. [0 marks]

(ii) The average power delivered to a series RLC circuit at frequency ω is given by

$P_{av} = \frac{1}{2} I_0^2 R \cos \phi$. Show that the peak current can be written as

$I_0 = \frac{V_0}{\sqrt{R^2 + (X_L - X_C)^2}}$, where ω is the operating frequency of the circuit and ω_0 is the resonance frequency. Also show that the phase angle can be expressed as

$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$. [4 marks]

(b) (i) What is it meant by the Quality factor (Q) of a **circuit**? [06 marks]

(ii) Explain how the quality factor is related to the response characteristics of a receiver. Which variable most strongly determines the quality **factor**? [0 marks]

(iii) "At frequencies above resonant frequency, impedance is inductive" State whether the above statement is true or false. **Explain** [10 marks]

End.