

**RAJARATA UNIVERSITY OF SRI LANKA**  
**FACULTY OF APPLIED SCIENCES**

Bachelor of Science in Applied Sciences  
Second Year - Semester I Examination – July/August 2023

**PHY 2103 – ELECTRONICS I**


**Time: One (01) hour**

---

**Answer only two Questions.**  
Calculators will be provided.


---

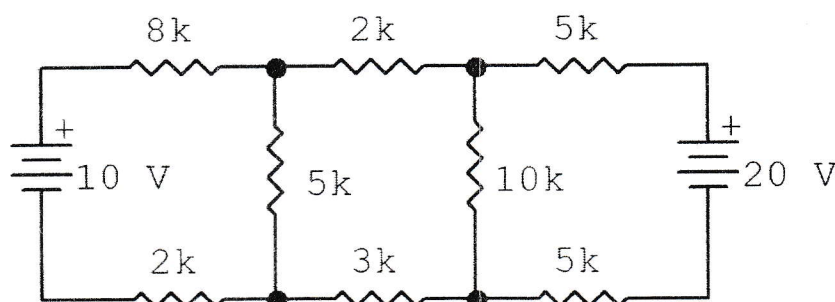1. a) Using the Kirchhoff's rules, determine the current through the 10V DC voltage source.



(05 marks)

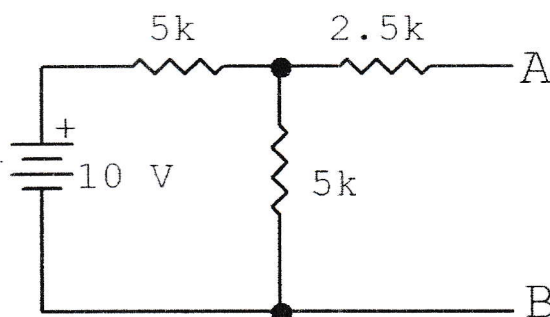- b) Using the Norton's theorem, draw Norton equivalent circuit for the following figure.




(05 marks)

- c) Explain using a diagram and the appropriate laws of physics, why an energy band is present in a bulk material instead of a single energy level.

(05 marks)

**Contd.**

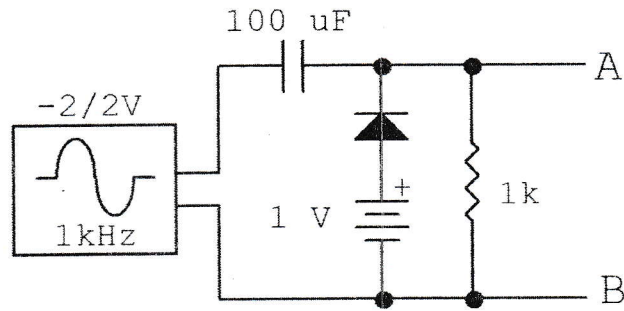- d) Using a plot, illustrate the output signal produced by the circuit shown in the figure below, for a 2V (peak) sinusoidal input signal.




(05 marks)

2. a) What are the three configurations of a bipolar junction transistor? State and discuss on voltage gain, current gain giving one application for each configuration.

(06 marks)

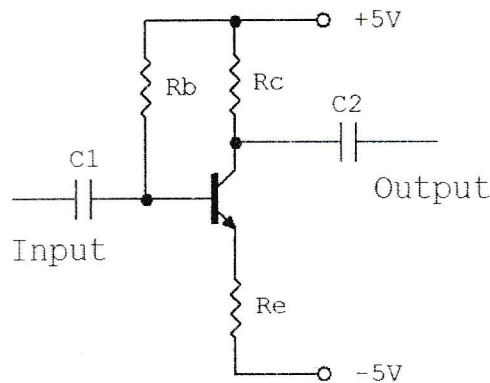
- b) Use the given fixed base biasing Transistor circuit to perform the following calculations.



- Choose a suitable collector voltage value for the  $V_c$  to design a class A amplifier for obtaining a sinusoidal output signal of 4V peak voltage.
- Calculate  $R_c$  for a 2 mA collector current.
- Calculate base current  $I_B$  when the current gain ( $\beta$ ) is 200.
- Determine a suitable value for  $R_E$  to bias the transistor into active region.
- Assuming transistor is made from Germanium, calculate suitable values for the  $R_B$ .
- What is the main disadvantage of fixed base biasing arrangement?
- Give one suggestion to avoid above-mentioned (part vi.) drawback.

(14 marks)

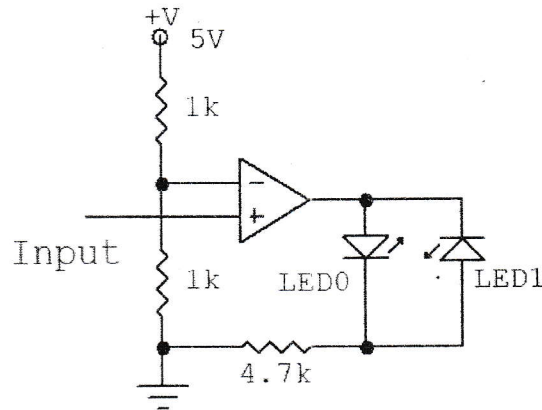3. a) What is the difference between positive and negative feedback of Op-amp circuits?  
(02 marks)
- b) Explain the functioning of an op-amp circuit shown below (supply voltage of the Op-amp is 5V and -5V).




(04 marks)

- c) Explain the deviation of an op-amp from the ideal behaviour based on its input/output impedances, open loop voltage gain, and the op-amp slew rate.

(06 marks)

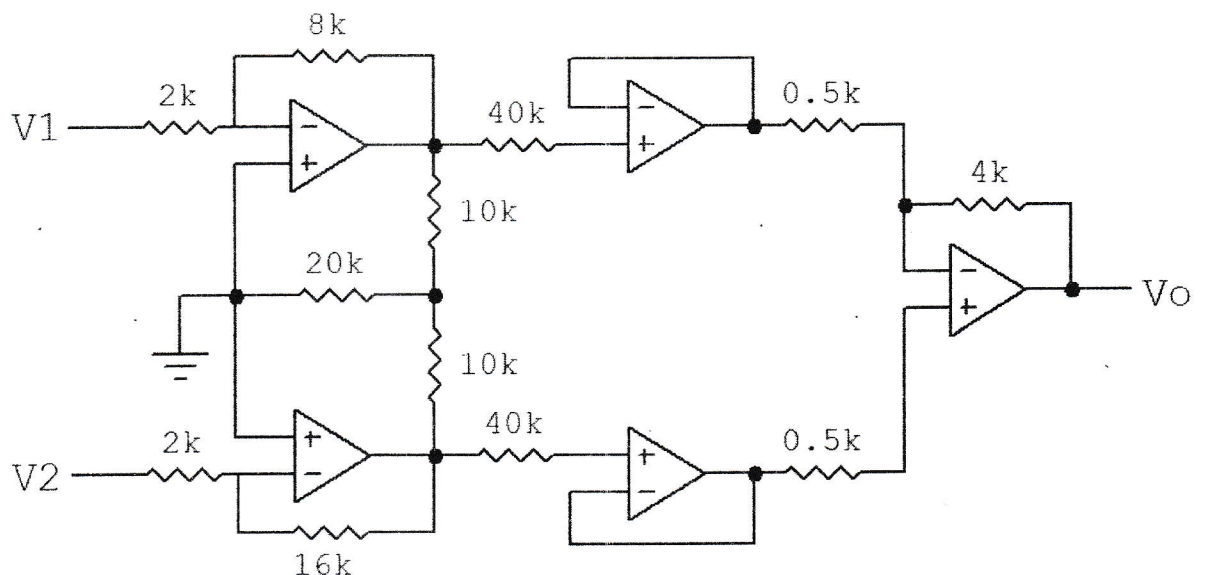- d) Using ideal Op Amp model, show that the output voltage of the following circuit is given by,  $V_o = 32V_1 - 72V_2$



(10 marks)

End.