



**RAJARATA UNIVERSITY OF SRI LANKA**  
**FACULTY OF APPLIED SCIENCES**

**B.Sc. Honors in Chemistry**  
**Third Year - Semester II Examination – July 2020**

**CHE 3222 – ELECTRONICS AND IT FOR CHEMISTS**

**Time: Two (2) hours**

**Answer all Questions**

1.
  - a)
    - i. What is the difference between a Microsoft Excel function and Excel formula? (10 marks)
    - ii. A user wishes to remove a Microsoft Excel spreadsheet from a workbook. What is the correct sequence of events that will do this? (10 marks)
  - b) What is a molecular editor software? (10 marks)
  - c)
    - i. Write down a short account of open source technology? (30 marks)
    - ii. What is Shell in a UNIX system? (20 marks)
    - iii. Explain the importance of directories in a UNIX system (10 marks)
    - iv. Write a command to list down file / folder lists alphabetically in a UNIX system? (10 marks)
  
2.
  - a)
    - i. Write down a short account of subject gateway (30 marks)
    - ii. What is a “search engine”? Briefly explain with examples (15 marks)
  - b) Assume that you have a protein pdb file called 2VDY.pdb and it is located on “C:\rasmol\” Write a rasmol script file that opens the pdb file, change background color as white, restrict the view to residues 230-250 in red color and display the possible disulfide bridges. (25 marks)

c) Explain the following rasmol commands


- i. set picking label
- ii. spacefill temperature
- iii. zap

(30 marks)

3.
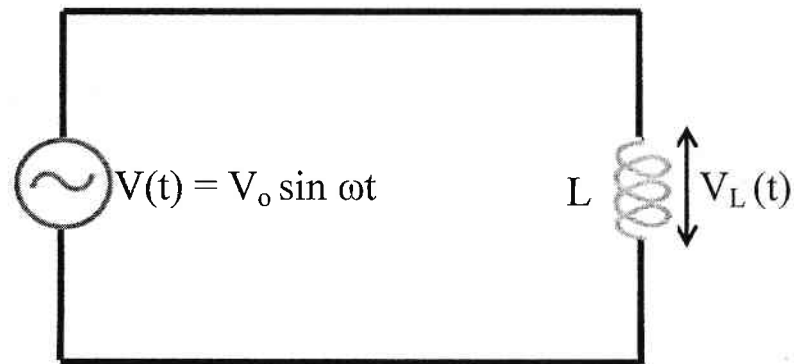
### Part I


Following circuit shows a purely inductive circuit with inductance  $L$  connected to an AC generator.



- a) Using Kirchhoff's rule show that the instantaneous current in the inductor is given by,  $I_L(t) = (\frac{V_{Lo}}{\omega L}) \sin(\omega t - \frac{\pi}{2})$ , where terms have their usual meaning.
- b) Sketch the time dependence of the current and the voltage across the inductor.
- c) Draw the Phasor diagram of the above circuit and comment on the phase difference between the current and the voltage.
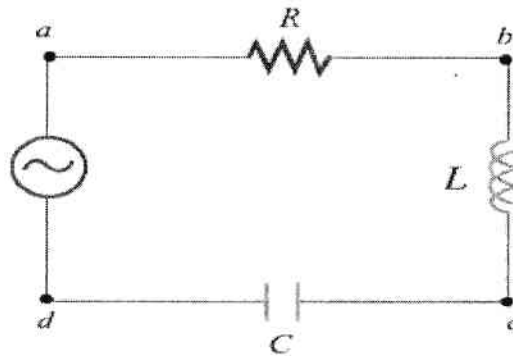
### Part II


Following diagram shows an LCR circuit with  $R = 40 \Omega$ ,  $L = 80 \text{ mH}$ ,  $C = 50 \mu\text{F}$  and an AC generator of  $V_C = (150 \text{ V}) \sin 100 t$ .



- Find the impedance of the circuit.
- Calculate the resonance frequency and the Q factor of the circuit.
- Calculate the maximum potential difference across points *b* and *d*.

(100 marks)

4.

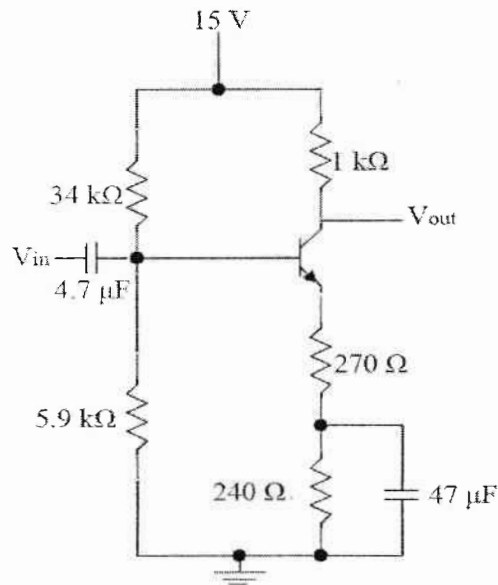**Part I**

- Find the values of Thevenin's voltage ( $V_{TH}$ ) and resistance ( $R_{TH}$ ), so that the circuit could be simplified to have a separate voltage source to the base terminal and a single base resistance.
- Sketch the load line of the circuit with short circuit current and open circuit voltage values.
- Find the Q – point of the circuit.

$$\beta = 200$$

**Part II**

- Construct a truth table for the following sum of product expression.  

$$A = xy\bar{z}t + xy'zt + xy'z't + x'yz't + x'yz't' + x'yzt' + x'y'z't'$$
- Find the minimal form of the above expression using Karnaugh maps.
- Draw the logic circuit.

replace by  
1

(100 marks)

-End-