



**RAJARATA UNIVERSITY OF SRI LANKA**  
**FACULTY OF APPLIED SCIENCES**

**B.Sc. (General) Degree in Applied Sciences**  
**Third Year - Semester I Examination – September / October 2019**

**PHY 3212 – ELECTRONICS II**

**Time: Two (02) hours**

- 
- **Answer all questions**
  - A non-programmable calculator is permitted.
  - All undefined symbols or terms appear below have their usual meanings.
- 

1. a) Express + 44 and – 62 as an 8 bit binary number in
  - i. sign magnitude
  - ii. 1's complement method
  - iii. 2's complement method

**(04 marks)**

b) In 16-bit 2's complement binary notation, add the maximum positive integer to the minimum negative integer. Express the answer in true binary.

**(06 marks)**

c) Convert the following decimal numbers to binary, multiply by partial products method, and divide by 2's complement method.

i. -36 x 64                      ii. 168 / (-14) **(08 marks)**

d) Convert the following binary numbers to gray code, and draw a logic diagram for 6 bits binary- to- gray- code converter.

i. 110010                      ii. 010101001 **(07 marks)**
2. a) Design a parity generation circuit for a 5-bit data (4-bit message with an odd parity bit) to be transmitted by a computer. Give the following for the parity generation.
  - i. the truth table, **(05 marks)**
  - ii. Karnaugh map, **(05 marks)**
  - iii. logic expression, and **(05 marks)**
  - iv. logic diagram using only XOR and XNOR gates. **(06 marks)**

b) State two practical advantages and disadvantages of using parity bits to detect errors.

**(04 marks)**

3. a) Explain the universal property of NOR gate. (06 marks)

- b) Use a Karnaugh map to find the minimum sum of products (SOP) form for the following expression.

$$f(A, B, C, D) = A \bar{B} \bar{C} D + A C \bar{D} + B \bar{C} D + \bar{A} B C \bar{D} \quad (05 \text{ marks})$$

- c) Use a Karnaugh map to find the minimum product of sums (POS) form for the following expression.

$$g(W, X, Y, Z) = (X + \bar{Y})(W + \bar{Z})(\bar{X} + \bar{Y} + \bar{Z})(W + X + Y + Z) \quad (05 \text{ marks})$$

- d) i. Convert the following POS expression to minimum SOP expression using a Karnaugh map.

$$f(A, B, C, D) = (\bar{A} + B)(\bar{A} + \bar{B} + \bar{C})(B + \bar{C} + D)(A + \bar{B} + C + \bar{D}) \quad (05 \text{ marks})$$

- ii. Draw the combinational logic circuit for the above minimum SOP expression in (d)(i). using only XNOR, AND and OR gates. (04 marks)

4. A code converter converts a BCD number ( $A_3A_2A_1A_0$ ) to excess 3 code ( $B_3B_2B_1B_0$ ) where  $A_0$  and  $B_0$  are LSBs.

- a) Give the truth table for the conversion. (05 marks)

- b) Obtain the SOP expressions for each bit of excess 3 code. (04 marks)

- c) Map the expressions in (b) on Karnaugh maps. (12 marks)

(Please mark the six invalid codes of BCD as don't cares (X)).

- d) Find the minimum SOP expressions. (04 marks)

(The don't cares (X) can only use to form groups if it simplifies logic. However there is no requirement to group all or any of the don't cares (X)).

---END---