



51

**RAJARATA UNIVERSITY OF SRI LANKA
FACULTY OF APPLIED SCIENCES**

**B.Sc. (General) Degree in Applied Sciences
First Year - Semester II Examination – February / March 2019**

COM 1308 – DIGITAL LOGIC DESIGN

Time: Three (03) hours

Instructions to Candidates:

1. This paper contains **SIX (06)** questions in **FOUR (04)** pages.
 2. All questions carry equal marks.
 3. Answer **ANY FIVE (05)** questions.
-
1. a. Elaborate the requirement to use truth tables in explaining the operation of a logic circuit.
(05 marks)
 - b. Explain the operation of following logic gates using truth tables.
 - i. NAND
 - ii. NOR
 - iii. OR
 - iv. X-NOR
 - v. X-OR(05 marks)
 - c. Using above truth tables, show how a NOT gate can be synthesized using other logic gates.
(05 marks)
 - d. Show that, $x + yz = (x + y) \cdot (x + z)$ using truth tables.
(05 marks)

2. a. State DeMorgan's theorem and prove it using truth tables.

(05 mark)

- b. Find the minimum sum-of-products expression for the function,

$$f = w\bar{x}\bar{y} + wxz + w\bar{x}y\bar{z}$$
 using algebraic manipulation.

(05 mark)

- c. "NAND and NOR gates are universal gates". Discuss this statement explaining how the basic logic gates are synthesized using either NAND or NOR gates.

(05 mark)

- d. Prove that,

$$(\bar{x} + \bar{y} + \bar{z}). (\bar{x} + y + \bar{z}). (x + y + \bar{z}). (x + y + z) = \bar{x}z + x\bar{y}$$

using Karnaugh Maps.

(05 mark)


3. a. A digital lock is controlled by three fingerprint scanners. The fingerprint scanner produces a signal when a defined fingerprint is identified. The lock opens when two persons present their fingerprints simultaneously. The lock will remain locked if all three persons press their fingers simultaneously. Design and implement a logic circuit to control the lock. Take the inputs from fingerprint scanners as f_1 , f_2 , and f_3 respectively.

(10 mark)

- b. Implement a full adder using NAND gates.

(10 mark)

 
4. a. The following circuit shows the logical implementation of a 2-to-1 multiplexer.



Construct a 4-to-1 multiplexer using these circuits as building blocks.

(05 mark)

 - b. A code converter is used to drive a 7-segment display according to the input from a decimal counter. In the figure, w_0, w_1, w_2 , and w_3 denote the inputs from decimal counter. Outputs from the code converter, $y_0 - y_6$, corresponds to each segment of the display.




Design and implement the logical circuit required to produce the output y_4 of the converter. (10 marks)

- c. **“Encoders are used to reduce the number of bits needed to represent given information”**. Discuss this statement giving appropriate examples. (05 marks)

5. a. Using appropriate circuit diagrams show that a simple latch has two stable states. (05 marks)

- b. Elaborate how edge triggering is achieved in Master-Slave configuration using D Flip-Flops. Use timing diagrams to explain the operation. (05 marks)

 - c. The following circuit shows a Master-Slave D Flip-Flop. Explain the use of the two signals X and Y.



(10 marks)

6. a. Design and implement a synchronous octal (divide-by-8) counter.

(20 marks)

---- End ----