



RAJARATA UNIVERSITY OF SRI LANKA  
FACULTY OF APPLIED SCIENCES

B. Sc (General) Degree in Information and Communication Technology  
First Year - Semester I Examination - June/July 2018

ICT 1303 – BASIC ELECTRONICS AND DIGITAL LOGIC DESIGN

Time: Three (03) hours

Instructions to Candidates:

1. This paper contains six (06) questions in three (03) pages.
2. Answer any five (05) questions.

1.

- a) Why do intrinsic semiconductors need to be doped before they are used in a diode?


(05 Marks)

- b) Discuss the rectification function of semiconductor diodes using suitable circuit diagrams.

(05 Marks)

- c) The following circuit shows a voltage doubler. Explain its operation using appropriate graphs of  $V_{ac}$  and  $V_{out}$ .

(10 Marks)

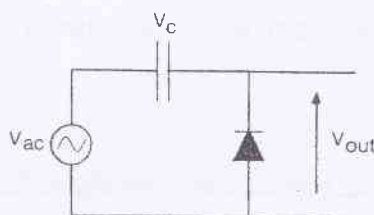

2.


- a) Explain the internal structure of a bipolar junction transistor and the purpose of doping different sections at different levels.

(10 Marks)


- b) "Common collector amplifiers have desirable properties for input and output stages".  
Discuss this statement. (05 Marks)
- c) Compare and contrast negative feedback and positive feedback (05 Marks)

3.

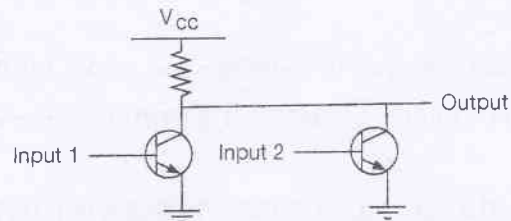- a) Explain the operation of the following logic circuit and name it. (05 Marks)



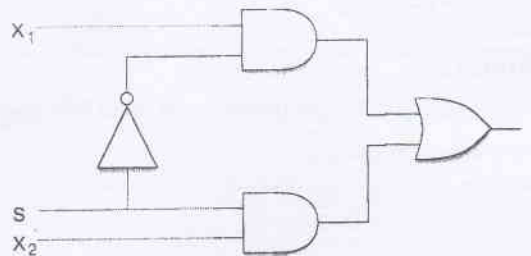- b) Identify the function of the following circuit and explain its uses. (10 Marks)



- c) Explain why it is always desirable to implement logic circuits using NAND and NOR gates. (05 Marks)


4.

- a) Design a logic circuit that would add 3 bits together. You are required to build the truth table and derive the logical function of the circuit from it. (10 Marks)
- b) Show that the above circuit can be reduced to two half adders and an OR gate. (10 Marks)

5.

- a) Using appropriate circuit diagrams show that a latch has two stable states. (05 Marks)

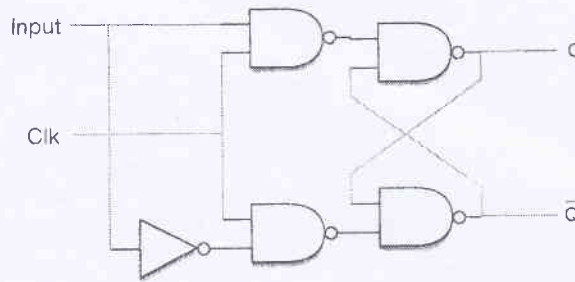- b) The following diagram shows the logic implementation of a flip-flop. Identify it and write down its characteristic table. (10 Marks)



- c) Briefly explain how master-slave flip-flops are used to achieve edge-triggering. (05 Marks)

6.

- a) Design a decimal up counter using JK flip-flops. (20 Marks)

- End -