



**RAJARATA UNIVERSITY OF SRI LANKA  
FACULTY OF APPLIED SCIENCES**

**B.Sc. (General) Degree in Applied Sciences  
Second - Year Semester I Examination – September /October 2019**

**PHY 2103 – ELECTRONICS I**

**Time: One (01) hour**

- 
- **Answer only two questions**
  - A non-programmable calculator is permitted.
  - All undefined symbols appear below have their usual meanings.
- 

1. a) Briefly explain the
    - i. built in potential of a p-n junction diode. **(10 marks)**
    - ii. forward biased and reverse biased characteristics of a p-n junction diode. **(05 marks)**b) What happens to the depletion region under different biased situations? **(10 marks)**  
c) How does the dynamic resistance of a p-n junction diode vary with the current? **(05 marks)**  
d) What distinguishes conductors, semiconductors and insulators in terms of the forbidden energy gap? **(10 marks)**  
e) What effect do added impurities have on semiconductor conductivity? **(10 marks)**
  2. a) Explain the action of the full-wave and half-wave rectifier circuits. **(10 marks)**  
b) Draw the input and output waveforms of the bridge rectifier circuit that has a capacitor filter with a load. **(10 marks)**  
c) Derive an expressions for the ripple voltage and the ripple factor of the circuit. **(10 marks)**
- continued...*


- d) Given that the supply voltage is 230 V (r.m.s.), the frequency is 50 Hz, capacitance of the capacitor is 1000  $\mu\text{F}$  and the load resistance is 1 k $\Omega$ , calculate the ripple voltage and the ripple factor.

(20 marks)

3. a) Describe the operation of an n-p-n transistor. (15 marks)

- b) The operating point of the circuit shown below is chosen such that  $I_C = 2 \text{ mA}$  and  $V_{CE} = 3 \text{ V}$ . Calculate the values of  $R_1$ ,  $R_2$  and  $R_E$  if  $R_C = 2.2 \text{ k}\Omega$ ,  $V_{CC} = 9 \text{ V}$  and  $\beta = 50$ . Assume that the barrier  $V_{BE} = 0.6 \text{ V}$  and  $I_1 = 10 I_B$

(35 marks)

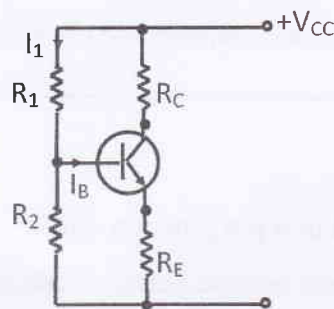

--- END ---