



RAJARATA UNIVERSITY OF SRI LANKA
FACULTY OF APPLIED SCIENCES


B.Sc. (General) Degree in Applied Sciences
 Second Year – Semester I Examination – Oct/ Nov 2015

PHY2103–Electronics

Answer All Questions.

Time allowed: $1\frac{1}{2}$ hours

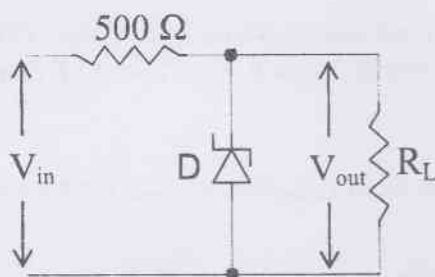
1. The Zener diode in the circuit has following characteristics: 7.0 V rating at 10 mA, $r_z = 20\ \Omega$ and $I_{zk} = 0.2\text{ mA}$.



- Find V_{zo} of the Zener diode.
- Find V_{out} with no load (no R_L) and $V_{in} = 10\text{ V}$.
- Find the change in output voltage (V_{out}), if the input voltage (V_{in}) fluctuate by $\pm 1\text{ V}$.
- The Line Regulation of a regulator circuit is defined by the ratio of the change in output voltage to the change in input voltage ($\frac{\Delta V_{out}}{\Delta V_{in}}$). Find the Line Regulation of the above circuit.
- Find the change in output voltage (V_{out}), resulting from connecting a load of $2\text{ k}\Omega$ ($R_L = 2\text{ k}\Omega$) to the circuit.

(35 Marks)

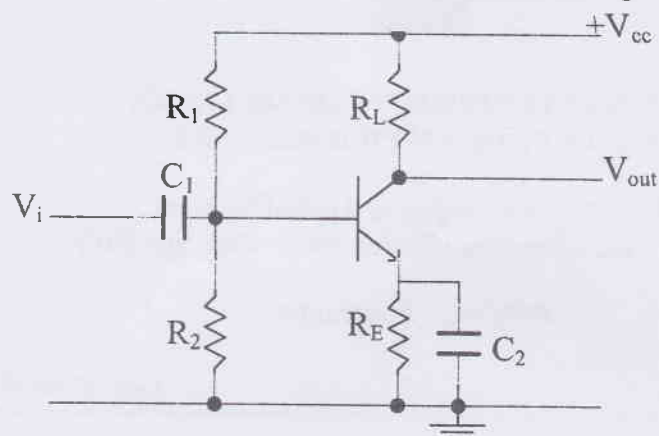2. Following circuit diagram shows a common-emitter configuration of an **npn** transistor.




- Using Thevenin's theorem simplify the above circuit to have one base resistor (R_{TH}) and one base power source (V_{TH}). Derive equations for R_{TH} and V_{TH} .
- Derive equations for open circuit voltage ($V_{CE(max)}$) and short circuit current ($I_{C(max)}$). If $R_1 = R_2 = 150 \Omega$, $R_L = R_E = 500 \Omega$, $V_{BE} = 0.7 V$, $V_{CC} = 12 V$ and $\beta = 100$, calculate the $I_{C(max)}$ and $V_{CE(max)}$.
- Sketch the load line and mark the $I_{CE(max)}$ and $V_{CE(max)}$ for the above circuit.
- Find the **Q-point** of the circuit.
- Show that the **Q - point** of the above circuit is independent of the change in β .


(35 Marks)

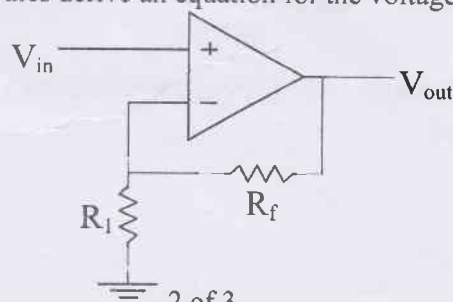3. Operational Amplifiers (Op-Amp) are a class of high gain DC coupled amplifiers with two differential inputs and one output terminal.


- State two golden rules of an ideal Op Amp.
- Using above mentioned rules derive an equation for the voltage gain of the following non-inverting amplifier.



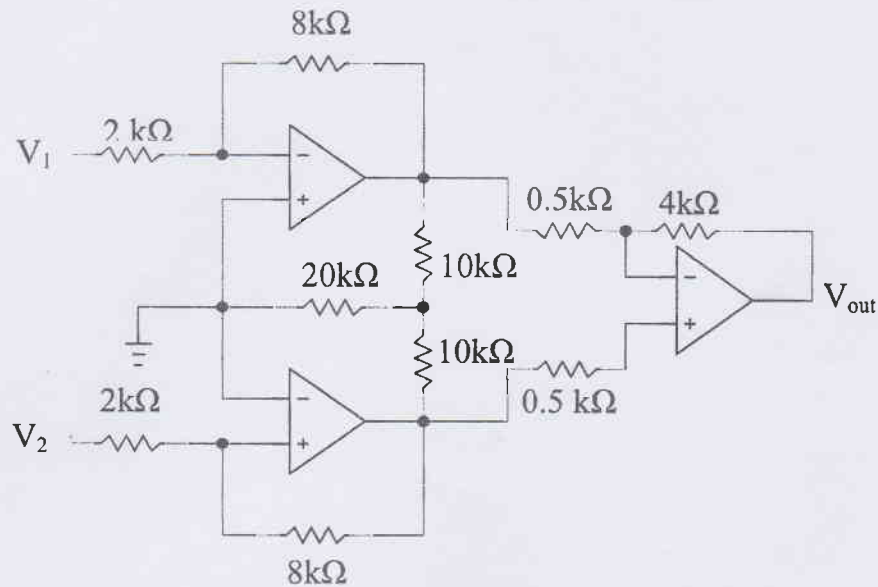- c. Following circuit has two inputs (V_1 and V_2) and one output (V_{out}). Derive an equation for the output voltage (V_{out}) in terms of V_1 and V_2 . (Assume all the Op-Amps are ideal)



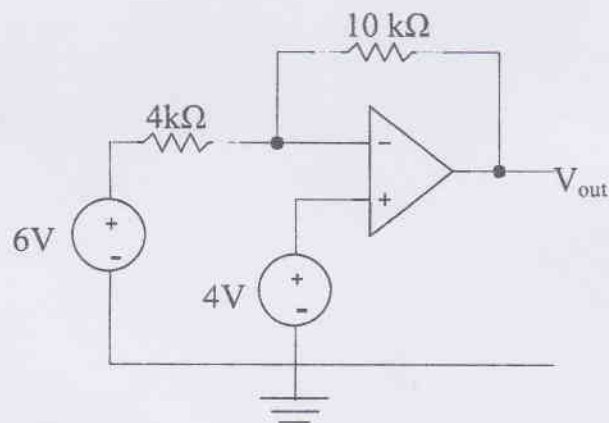- d. Calculate the V_{out} of the following inverted circuit.



(30 Marks)