



RAJARATA UNIVERSITY OF SRI LANKA
FACULTY OF APPLIED SCIENCES
B.Sc. (Information and Communication Technology) Degree
First Year Semester I Examination May / June 2016

ICT1303 – BASIC ELECTRONICS AND DIGITAL LOGIC DESIGN

Answer any five (05) questions

Time: 3 hours


- 01 a. **“In an intrinsic semiconductor, the number of holes is equal to the number of free electrons”**. Discuss the effect of adding an (trivalent or pentavalent) impurity to an intrinsic impurity.

(05 Marks)

- b. Discuss the operation of an ideal diode giving its transfer function. Discuss both forward and reverse biased operations.

(10 Marks)

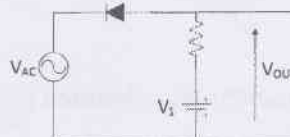- c. Explain the operation of this circuit drawing V_{AC} and V_{OUT} , and identify its operation.



(05 Marks)


- 02 a. Discuss the construction of a bipolar junction transistor giving necessary illustrations. Elaborate the effect of different levels of doping in different regions.

(10 Marks)

- b. **“An electronic circuit is desirable to have a very high input impedance and a very low output impedance”**. Discuss this statement.

(05 Marks)

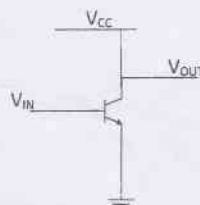
- c. Explain the operation of the given circuit when V_{IN} is 0 V and 3.5 V. Assume that V_{CC} is 5V.



(05 Marks)

- 03 a. "Field-effect transistors are called *unipolar* transistors". Discuss why. (05 Marks)

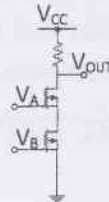- b. Explain the operation of the given circuit. Assume that both V_A and V_B are either 0 V or 5 V.




(05 Marks)

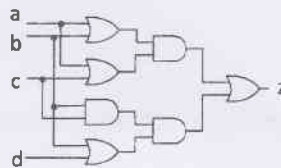- c. Elaborate the differences between constructions of *enhancement* and *depletion* types of Metal Oxide Semiconductor Field Effect Transistors (MOSFETs).

(10 Marks)

- 04 a. Write down the Boolean function of the given circuit.



(05 Marks)


- b. Simplify the function you obtained (in part a) above using a Karnaugh map. (10 Marks)

- c. Draw the circuit diagram of the simplified circuit. (05 Marks)

- 05 a. Draw the logic implementations of an S-R flip-flop and a J-K flip-flop and discuss the differences in their behavior. (05 Marks)

- b. Draw the circuit diagram of a J-K flip-flop and write down its characteristic table. (05 Marks)

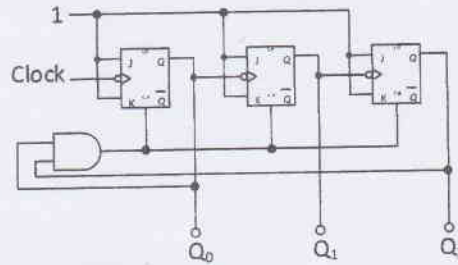- c. Explain the operation of the given sequential circuit using a timing diagram. Name the circuit considering its operation.



(10 Marks)

- 06 a. In Binary-Coded Decimal (BCD) representation, each decimal digit is encoded into a binary number separately. How many flip-flops are required to fabricate a divide-by-10 (MOD-10) BCD counter? Elaborate your answer using appropriate calculations.

(05 Marks)

- a. Elaborate the difference between synchronous and asynchronous counters. You may use illustrations as appropriate.

(05 Marks)

- c. Explain the steps involved in synchronous counter design using an appropriate example.

(10 Marks)

- 07 a. A grayscale counter counts numbers where two successive numbers differ only in one bit (e.g. $00 \rightarrow 01 \rightarrow 11 \rightarrow 10 \rightarrow 00$). Design an asynchronous divide-by-12 (MOD-12) grayscale counter.

(20 Marks)

- End of Paper -